

EECS151/251A

Introduction to Digital Design and ICs

Lecture 3 – Metrics & Verilog Sophia Shao



LICKING COUNTY, Ohio, Jan. 21, 2022 – Intel today announced plans for an initial investment of more than \$20 billion in the construction of two new leading-edge chip factories in Ohio. The investment will help boost production to meet the surging demand for advanced semiconductors, powering a new generation of innovative products from Intel and serving the needs of foundry customers as part of the company's [IDM 2.0 strategy](#). To support the development of the new site, Intel pledged an additional \$100 million toward partnerships with educational institutions to build a pipeline of talent and bolster research programs in the region.

<https://www.intel.com/content/www/us/en/newsroom/news/intel-announces-next-us-site-landmark-investment-ohio.html>

Review


- The design process involves traversing the layers of specification, modeling, architecture, RTL design and physical implementation.
- Digital systems implement a set of Boolean equations





- **Metrics:**
 - **Functionality and Robustness**
 - **Cost**
 - **Performance**
 - **Power and Energy**
- **Verilog!**
 - **Overview**
 - **Combinational Logic**

Design Tradeoffs

 - The desired functionality can be implemented with different performance, power or cost targets




Beneath the Digital Abstraction

  

- Logic gate interpret its inputs as 0s(Low) and 1s(High).
- Noise: unwanted variations of voltages and currents in digital circuits.
- Logic levels:
 - Mapping a continuous voltage onto a discrete binary logic variable
 - Low (0): $[0, V_L]$
 - High (1): $[V_H, V_{DD}]$
 - V_L V_H : nominal voltage levels



Noise Margins

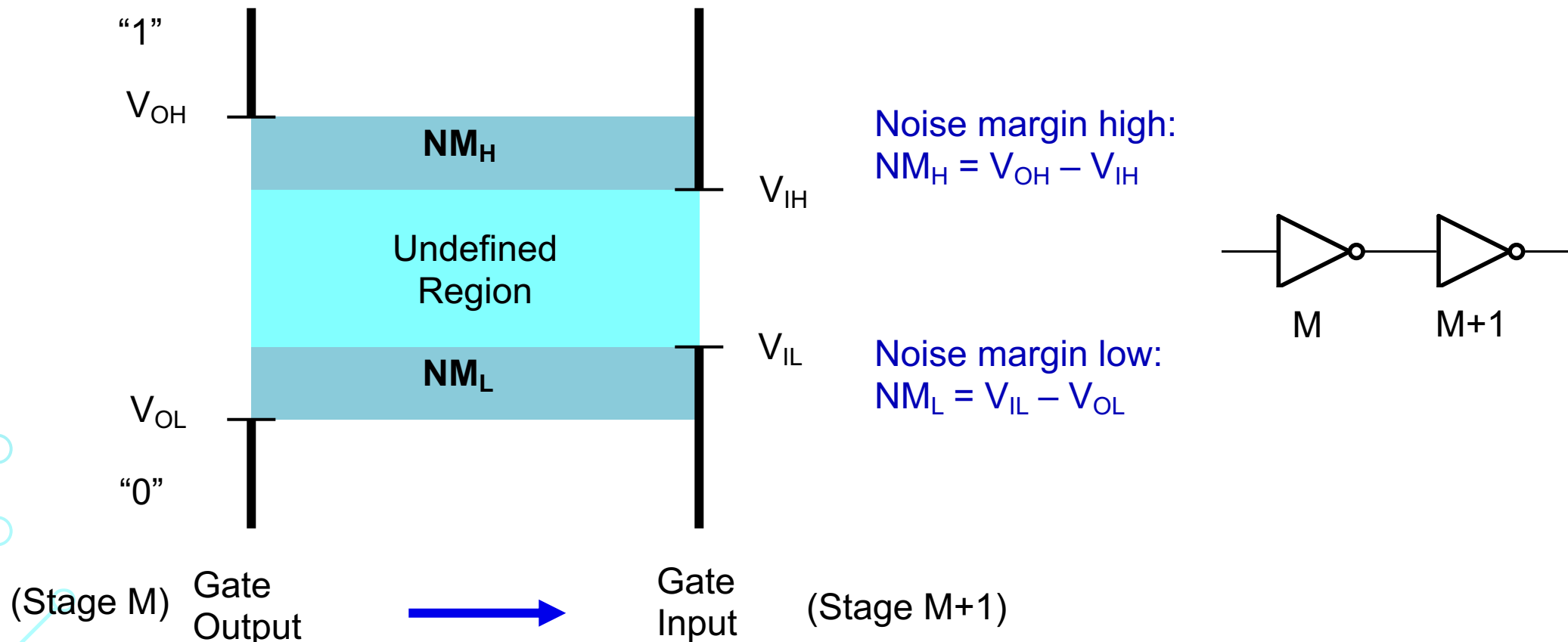- A measure of the sensitivity of a gate to noise.
- Represent the levels of noise that can be sustained when gates are cascaded.
- The amount of **noise** that could be added to a **worst-case output** so that the signal can still be interpreted correctly as a **valid input**.




Voltage Transfer Characteristic

  
- Describes the output voltage as a function of the input voltage.
- To choose logic levels \rightarrow slope = -1 \rightarrow maximize noise margin



a) Ideal

 


b) Real

 

Regenerative Property

 - Ensures that a **disturbed** signal gradually **converges back** to one of the **nominal voltage levels** after passing through a number of logical stages.
- Look for a sharp transition in voltage transfer characteristics.



Cost

- Non-recurring engineering (NRE) costs
 - Fixed, one-time cost to research, design, and verify a new piece of HW.
 - Amortized over all units shipped
 - E.g. \$20M in development adds \$.20 to each of 100M units
- Recurring costs
 - Cost to manufacture, test and package a unit
 - Processed wafer cost is ~10k (around 16nm node) which yields:
 - 1 Cerebras chip
 - 50-100 large FPGAs or GPUs
 - 200 laptop CPUs
 - >1000 cell phone SoCs


$$\text{cost per IC} = \text{variable cost per IC} + \frac{\text{fixed cost}}{\text{volume}}$$

$$\text{variable cost} = \frac{\text{cost of die} + \text{cost of die test} + \text{cost of packaging}}{\text{final test yield}}$$

Die Yield


Wafer

Single die

 


$$\text{Die cost} = \frac{\text{Wafer cost}}{\text{Dies per wafer} \times \text{Die yield}}$$
 
$$\text{Die Yield} = \frac{\text{No. of good chips per wafer}}{\text{Total number of chips per wafer}} \times 100\%$$




Defects

Yield = 0.25

 


Yield = 0.76

 



Performance

- Throughput
 - Number of tasks performed in a unit of time (operations per second)
 - E.g. Google TPUv3 board performs 420 TFLOPS (10^{12} floating-point operations per second, where a floating-point operation is BFLOAT16)
 - Watch out for 'op' definitions – can be a 1-b ADD or a double-precision FP add (or more complex task)
 - Peak vs. average throughput
- Latency
 - How long does a task take from start to finish
 - E.g. facial recognition on a phone takes 10's of ms
 - Sometime expressed in terms of clock cycles
 - Average vs. 'tail' latency

 


Digital Logic Delay

- Changes at the inputs do not instantaneously appear at the outputs
 - There are finite resistances and capacitances in each gate...
- Propagation delay t_p of a logic **gate**:
 - How quickly its output responds to a change at its inputs.
 - Defined as 50% transition points of the input and output waveforms.
 - High-to-low transition: t_{pHL}
 - Low-to-high transition: t_{pLH}
- Rise and fall times t_r t_f
 - For individual **signals**
 - How fast a signal transits
 - 10% - 90%

  

Digital Logic Timing

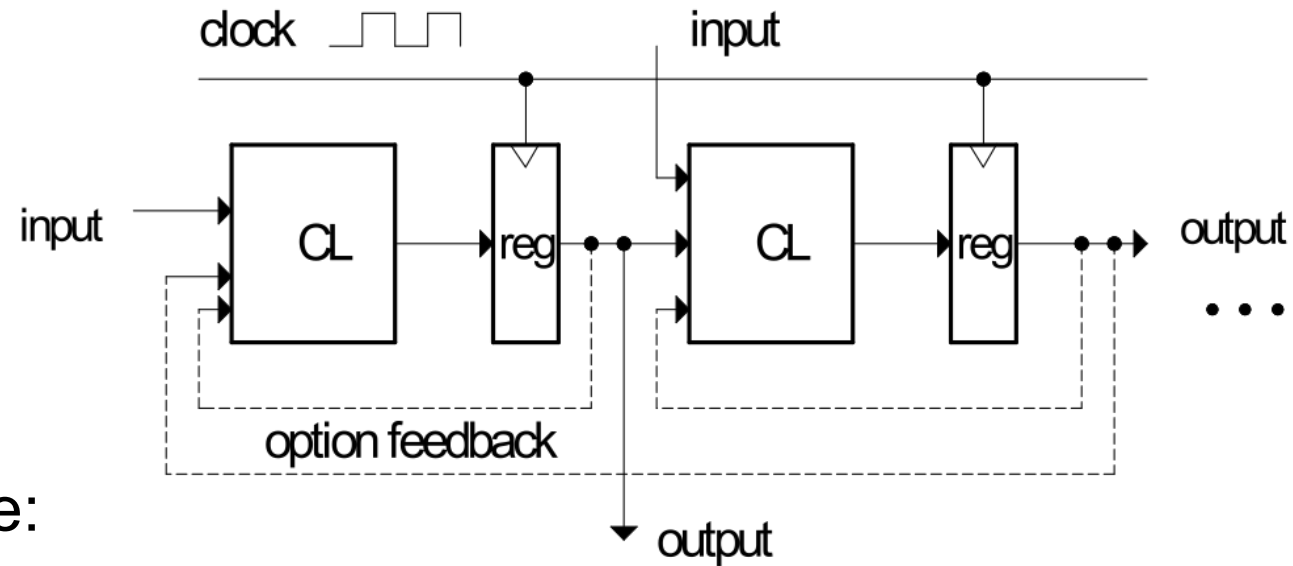
- The longest propagation delay through CL blocks sets the maximum achievable clock frequency.
 - Also need to consider register!



- To increase clock rate:
 - Find the longest path
 - Make it faster

Energy and Power

- Energy (in joules (J))
 - Needed to perform a task
 - Add two numbers or fetch a datum from memory
 - Active and standby
 - Battery stores certain amount of energy (in $Ws = J$ or Wh)
 - That is what utility charges for (in kWh)
- Power (in watts (W))
 - Energy dissipated in time ($W = J/s$)
 - Peak power vs average power
 - Sets cooling requirements
 - Heat spreader, size of a heat sink, forced air, liquid, ...

 

Liquid

Administrivia

- Lab 1 starts this week!
 - Complete Lab 1 on your own and ask for help in office hours.
- Homework 1 this week, due next Friday
 - Start early.
- Discussion 1 starts this week.
 - Know your classmates.



- **Metrics:**
 - **Functionality and Robustness**
 - **Cost**
 - **Performance**
 - **Power and Energy**
- **Verilog!**
 - **Overview**
 - **Combinational Logic**

Hardware **Description** Languages

Verilog:

- Simple C-like syntax for structural and behavior hardware constructs
- Mature set of commercial tools for synthesis and simulation
- Used in EECS 151 / 251A

VHDL:

- Semantically very close to Verilog
- More syntactic overhead
- Extensive type system for “synthesis time” checking

System Verilog:

- Enhances Verilog with strong typing along with other additions

BlueSpec:

- Invented by Prof. Arvind at MIT
- Originally built within the Haskell programming language
- Now available commercially: bluespec.edu

Chisel:


- Developed at UC Berkeley
- Used in CS152, CS250
- Available at: chisel.eecs.berkeley.edu

Verilog: Brief History

- Originated at Automated Integrated Design Systems (renamed Gateway) in 1985. Acquired by Cadence in 1989.
 - Invented as simulation language. Synthesis was an afterthought. Many of the basic techniques for synthesis were developed at **Berkeley** in the 80's and applied commercially in the 90's.
 - Around the same time as the origin of Verilog, the US Department of Defense developed VHDL (A double acronym! VSIC (Very High-Speed Integrated Circuit) HDL). Because it was in the public domain it began to grow in popularity.
 - Afraid of losing market share, Cadence opened Verilog to the public in 1990.
- Verilog is the language of choice of Silicon Valley companies, initially because of high-quality tool support and its similarity to C-language syntax.
- VHDL is still popular within the government, in Europe and Japan, and some universities.
- Most major CAD frameworks now support both.

Logic Synthesis

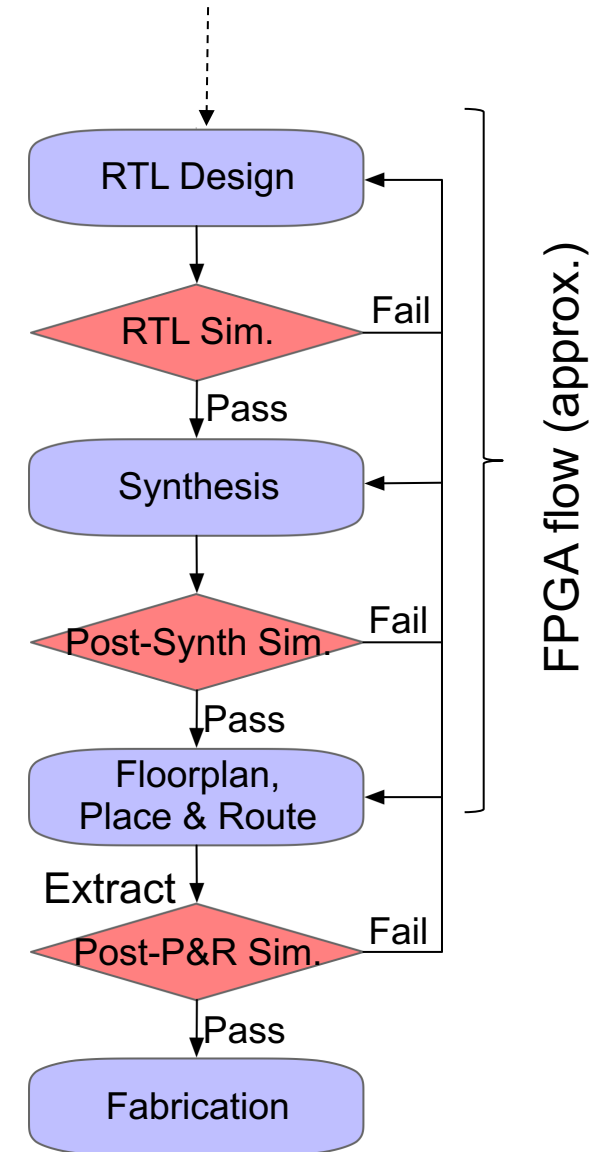- Verilog and VHDL started out as simulation languages but soon programs were written to automatically convert Verilog code into low-level circuit descriptions (netlists).
- Synthesis converts Verilog (or other HDL) descriptions to an implementation using technology-specific primitives:
 - For FPGA: LUTs, FlipFlops, and BRAMs.
 - For ASICs: standard cells and memory macros.



Verilog Introduction

- A module definition describes a component in a circuit
- Two ways to describe module contents:
 - **Structural Verilog**
 - List of sub-components and how they are connected
 - Just like schematics, but using text
 - tedious to write, hard to decode
 - You get precise control over circuit details
 - May be necessary to map to special resources of the FPGA/ASIC
 - **Behavioral Verilog**
 - Describe what a component does, not how it does it
 - Synthesized into a circuit that has this behavior
 - Result is only as good as the tools
- Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).

Verilog Modules and Instantiation


- Modules define circuit components.
- Instantiation defines hierarchy of the design.

```
      name      port list
module addr_cell (a, b, cin, s, cout);
  keywords  input  a, b, cin;
            output s, cout;
            module body
endmodule
            port declarations (input,
                               output, or inout)

module adder (A, B, S);
  Instance of addr_cell
  addr_cell ac1 ( ... connections ... );
endmodule
```


Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

Structural Model - XOR example

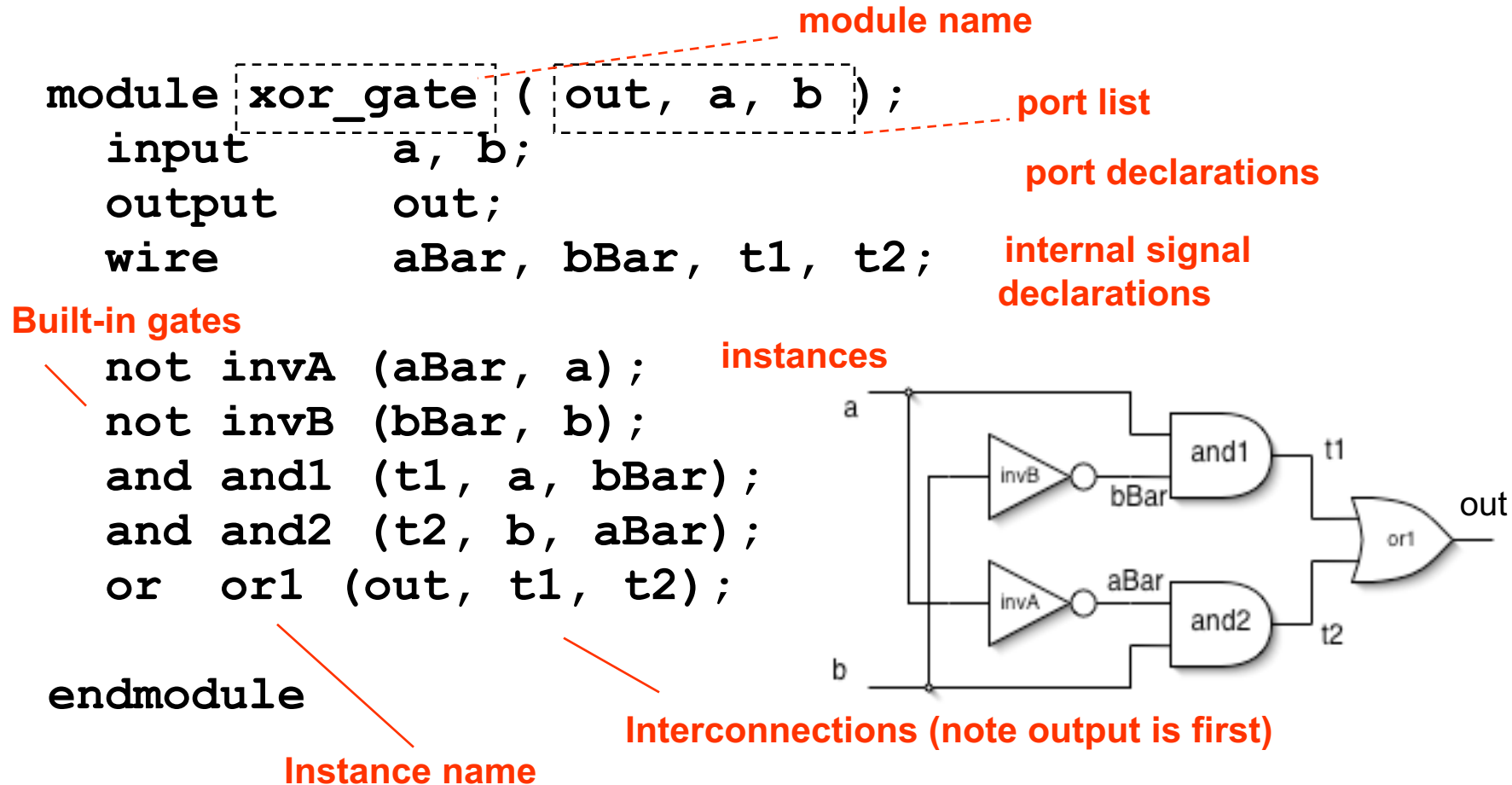

- Notes:
 - The instantiated gates are not “executed”. They are active always.
 - xor gate already exists as a built-in (so really no need to define it).
 - Undeclared variables assumed to be wires. Don’t let this happen to you!

Instantiation, Signal Array, Named ports

 

a) 4-input mux symbol

b) 4-input mux implemented with 2-input muxes

```
/* 2-input multiplexor in gates */  
module mux2 (in0, in1, select, out);  
    input in0,in1,select;  
    output out;  
    wire s0,w0,w1;  
    not (s0, select);  
    and (w0, s0, in0),  
        (w1, select, in1);  
    or (out, w0, w1);  
endmodule // mux2
```

```
module mux4 (in0, in1, in2, in3, select, out);
```

```
    input in0,in1,in2,in3;
```

```
    input [1:0] select; ----- Signal array. Declares select[1], select[0]
```

```
    output out;
```

```
    wire w0,w1;
```

```
    mux2
```

```
        m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
```

```
        m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
```

```
        m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
```

```
endmodule // mux4
```

Named ports. Highly recommended.

Simple Behavioral Model

```
module foo (out, in1, in2);  
  input      in1, in2;  
  output     out;
```

```
    assign out = in1 & in2;
```

```
endmodule
```

“continuous assignment”

**Connects out to be the logical
“and” of in1 and in2.**


Short-hand for explicit instantiation of bit-wise “and” gate (in this case).

The assignment continuously happens, therefore any change on the rhs is reflected in `out` immediately (except for the small delay associated with the implementation of the practical &).

Not like an assignment in C that takes place when the program counter gets to that place in the program.


Example - Ripple Adder

```
module FullAdder(a, b, ci, r, co);  
    input a, b, ci;  
    output r, co;  
  
    assign r = a ^ b ^ ci;  
    assign co = a&ci | a&b | b&cin;  
  
endmodule
```

 

```
module Adder(A, B, R);  
    input [3:0] A;  
    input [3:0] B;  
    output [4:0] R;
```
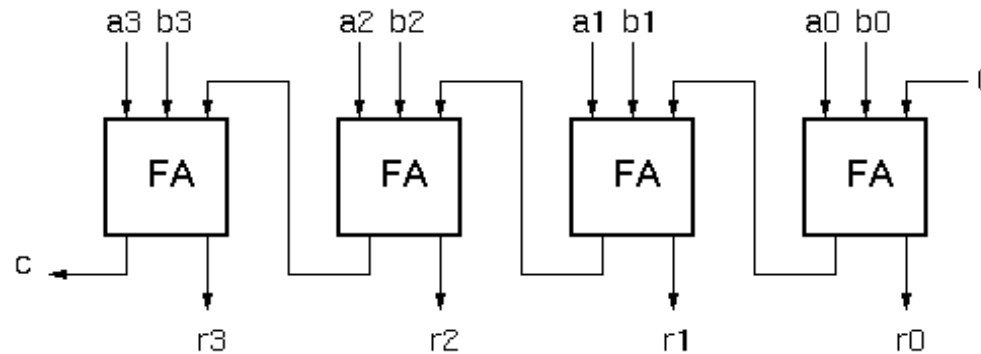
```
    wire c1, c2, c3;  
    FullAdder  
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
endmodule
```



Verilog Operators & Logic Values

Verilog Operator	Name	Functional Group
[]	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{ }	concatenation	Concatenation
{ { } }	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Continuous Assignment Examples

```
wire [3:0] A, X, Y, R, Z;  
wire [7:0] P;  
wire r, a, cout, cin;
```

```
assign R = X | (Y & ~Z);
```

use of bit-wise Boolean operators

```
assign r = &X;
```

example
reduction
operator

```
assign R = (a == 1'b0) ? X : Y;
```

conditional operator

```
assign P = 8'hff;
```

example constants

```
assign P = X * Y;
```

arithmetic operators (use with care!)

```
assign P[7:0] = {4{X[3]}, X[3:0]};
```

(ex: sign-extension)

```
assign {cout, R} = X + Y + cin;
```

bit field concatenation

```
assign Y = A << 2;
```

bit shift operator

```
assign Y = {A[1], A[0], 1'b0, 1'b0};
```

equivalent bit shift

Review

- Design metrics:
 - Functionality and robustness:
 - Cost
 - Performance
 - Power and Energy
- Verilog
 - Hardware description language: describe hardware!
 - Logic synthesis: Verilog -> Gate-level netlists
 - Used in both ASIC and Verilog
 - Assign statement